
 


David Strube - dstrube3@gatech.edu
OMCS6603 - VIP - Lab 1

 Here is a screenshot of the waveform viewer before I made any modifications



Here is a screenshot of the waveform viewer after I made some modifications



Here are the edits I made:

In the Verilog code, I changed this:

```
if (down)
    count <= count - 1;
else
    count <= count + 1;
```

to this:

```
if (down)
    count <= count - 2;
else
    count <= count + 2;
```

In the Testbench code, I changed the lines specifying the repeat count from 5 to 10. For example:

```
repeat (10) @(posedge clk);
&
for (int i = 0; i < 10; i++) begin
```

See below for the complete Verilog code and Testbench code:

design.sv:

```
module counter_ud
    #(parameter WIDTH = 4)
    (
```

```

input                clk,
input                rstn,
input wire [WIDTH-1:0] load,
input                load_en,
input                down,
output               rollover,
output reg [WIDTH-1:0] count
);

always @ (posedge clk or negedge rstn) begin
    if (!rstn)
        count <= 0;
    else
        if (load_en)
            count <= load;
        else begin
            if (down)
                count <= count - 2;
            else
                count <= count + 2;
        end
    end

    assign rollover = &count;

endmodule

```

testbench.sv:

```

//-----
// Author   : Admin, ChipVerify
// Website  : www.chipverify.com
//-----

interface cnt_if #(parameter WIDTH = 4) (input bit clk);
    logic                rstn;
    logic                load_en;
    logic [WIDTH-1:0] load;
    logic [WIDTH-1:0] count;
    logic                down;
    logic                rollover;

```

```

endinterface

module tb;
    reg clk;

    // TB Clock Generator used to provide the design
    // with a clock -> here half_period = 10ns => 50 MHz
    always #1 clk = ~clk;

    cnt_if    cnt_if0 (clk);
    counter_ud c0 (    .clk        (cnt_if0.clk),
                      .rstn        (cnt_if0.rstn),
                      .load        (cnt_if0.load),
                      .load_en     (cnt_if0.load_en),
                      .down        (cnt_if0.down),
                      .rollover    (cnt_if0.rollover),
                      .count       (cnt_if0.count));

    initial begin
        bit load_en, down;
        bit [3:0] load;

        $monitor("[%0t] down=%0b load_en=%0b load=0x%0h count=0x%0h
        rollover=%0b", $time, cnt_if0.down, cnt_if0.load_en, cnt_if0.load,
        cnt_if0.count, cnt_if0.rollover);

        // Initialize testbench variables
        clk <= 0;
        cnt_if0.rstn <= 0;
        cnt_if0.load_en <= 0;
        cnt_if0.load <= 0;
        cnt_if0.down <= 0;

        // Drive design out of reset after 5 clocks
        repeat (10) @(posedge clk);
        cnt_if0.rstn <= 1;

        // Drive stimulus -> repeat 5 times
        for (int i = 0; i < 10; i++) begin

```

```

// Drive inputs after some random delay
int delay = $urandom_range (1,30);
#(delay);

// Randomize input values to be driven
std::randomize(load, load_en, down);

// Assign tb values to interface signals
cnt_if0.load <= load;
cnt_if0.load_en <= load_en;
cnt_if0.down <= down;
end

// Wait for 5 clocks and finish simulation
repeat(10) @ (posedge clk);
$finish;
end

initial begin
    $dumpvars;
    $dumpfile("sth.vcd");
end
endmodule

/*
Simulation Log:
-----
ncsim> run
[0] down=0 load_en=0 load=0x0 count=0x0 rollover=0
[96] down=1 load_en=1 load=0x1 count=0x0 rollover=0
[102] down=0 load_en=0 load=0x9 count=0x0 rollover=0
[108] down=1 load_en=1 load=0x1 count=0x0 rollover=0
[110] down=1 load_en=1 load=0x1 count=0x1 rollover=0
[114] down=1 load_en=0 load=0xc count=0x1 rollover=0
[120] down=1 load_en=0 load=0x7 count=0x1 rollover=0
[130] down=1 load_en=0 load=0x7 count=0x0 rollover=0
[150] down=1 load_en=0 load=0x7 count=0xf rollover=1
[170] down=1 load_en=0 load=0x7 count=0xe rollover=0
[190] down=1 load_en=0 load=0x7 count=0xd rollover=0
Simulation complete via $finish(1) at time 210 NS + 0

```

```
./testbench.sv:66      $finish;  
ncsim> exit  
*/
```